
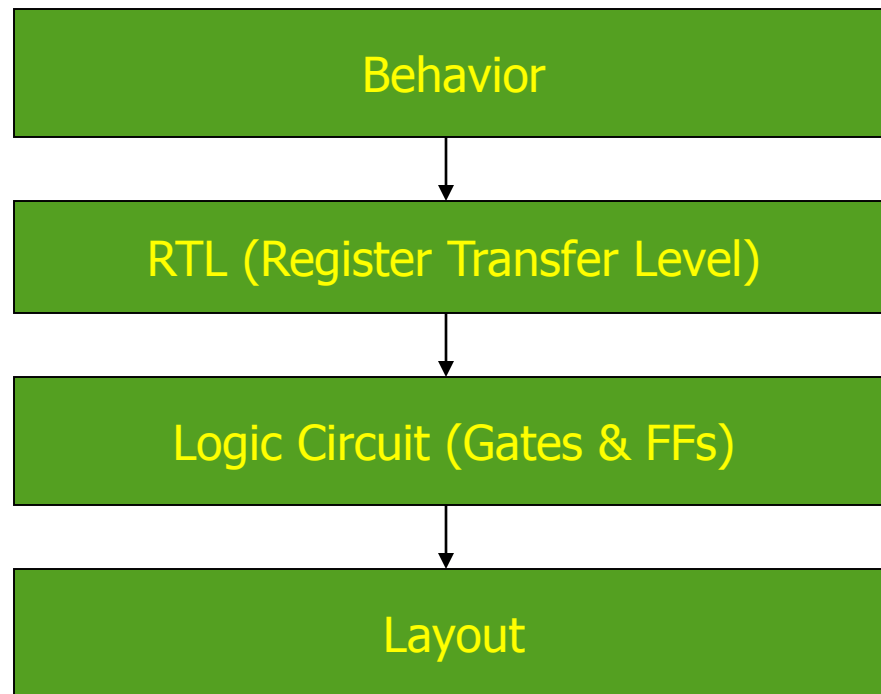


Hardware Description Language (HDL)


Digital Design Flow

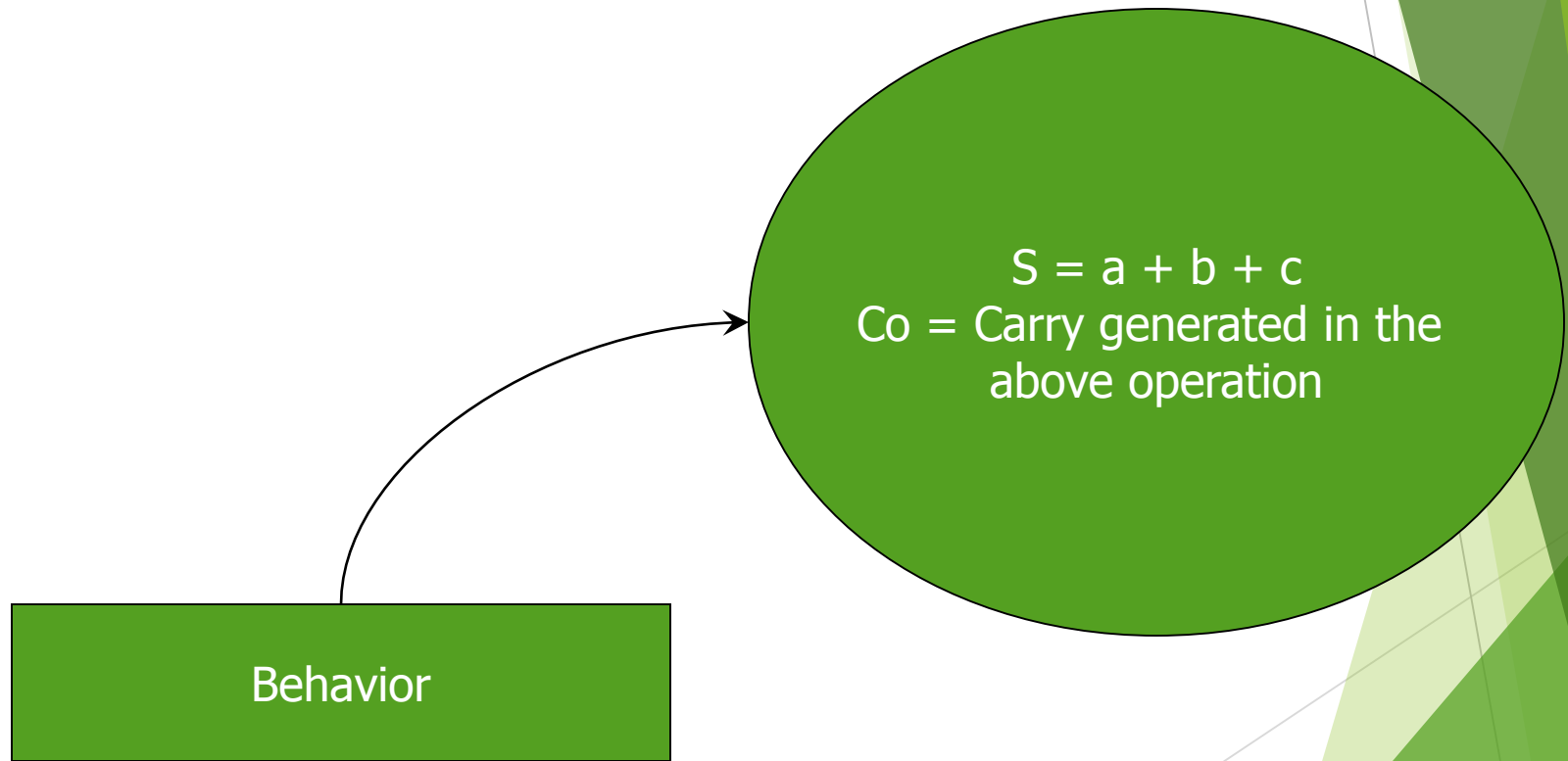


Abstractions in Digital IC Design - Example [1]



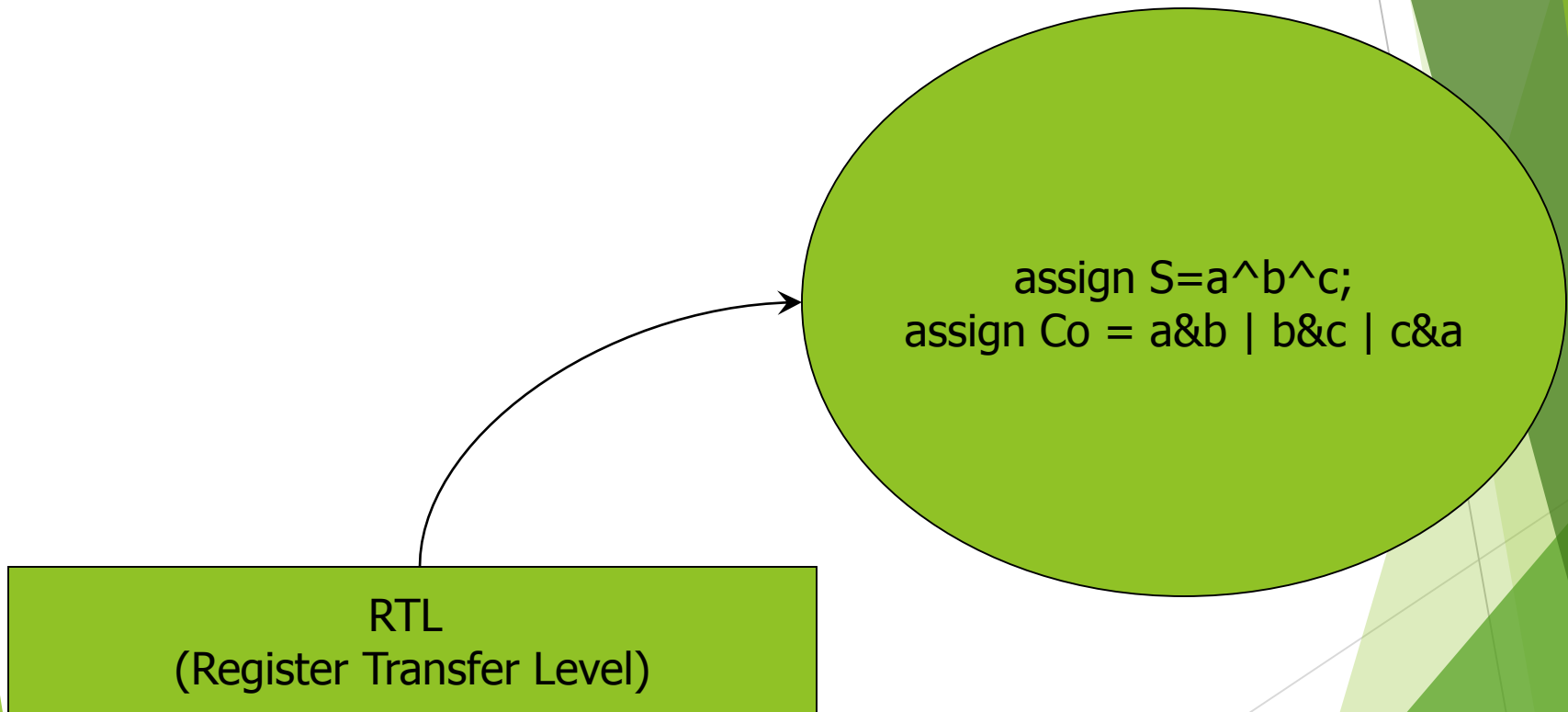Abstractions in Digital IC Design - Example [2]




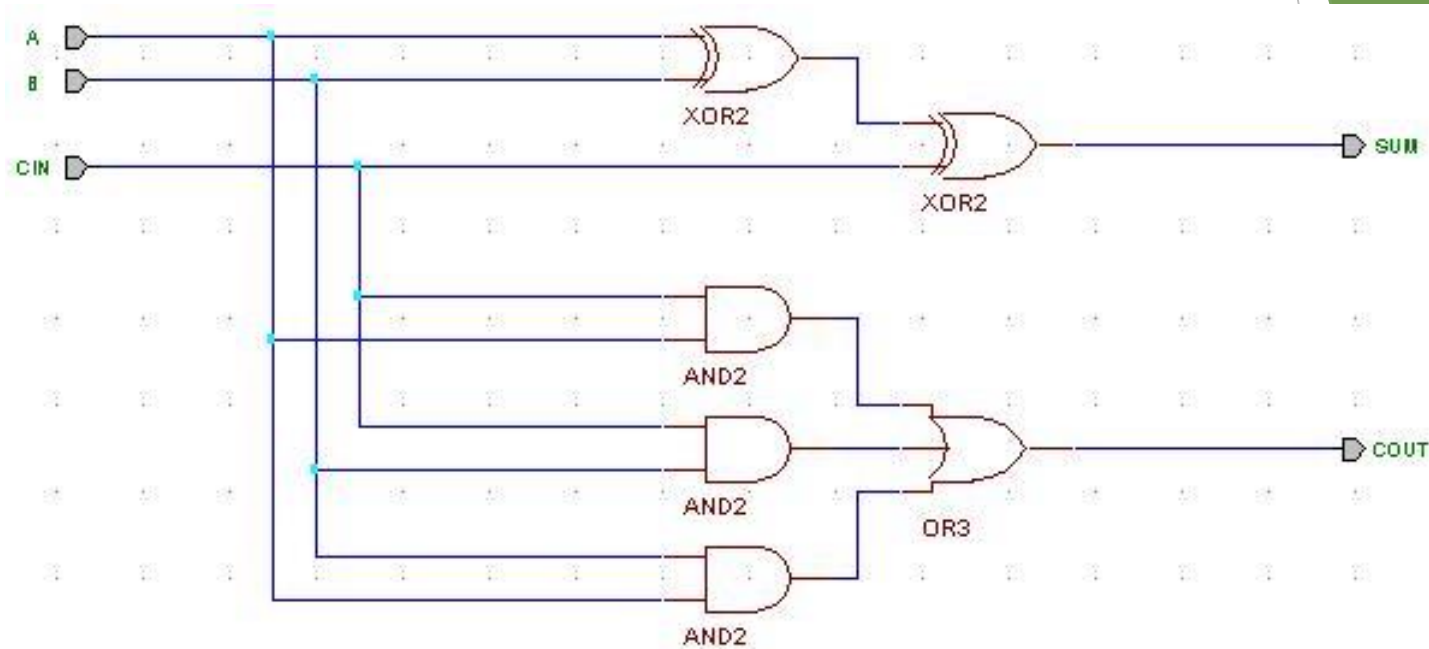Abstractions in Digital IC Design - Example [3]



Logic Circuit
(Gates & FFs)

Abstractions in Digital IC Design

 

Hardware Description Language (HDL)

- ▶ A Programming language used to describe **hardware**
- ▶ It resembles a programming language, but is specifically oriented to describing hardware structures and behaviors.
- ▶ The main difference:
 - ▶ traditional programming languages → mostly serial operations
 - ▶ HDLs → extensive parallel operations
- ▶ The most common use of a HDL is to provide an alternative to schematics.

Hardware Description Language (HDL)

- ▶ When a language is used for the above purpose (i.e. to provide an alternative to schematics), it is referred to as a *structural description* in which the language describes an interconnection of components.
- ▶ Such a structural description can be used as input to logic simulation just as a schematic is used.

Commercial HDLs...

- ▶ VHDL - VHSIC (Very High Speed Integrated Circuit) Hardware Description Language
- ▶ Verilog HDL - Verifying Logic HDL
- ▶ System C, System Verilog - very popular now

HDL Processing consists of two applications.

▶ - Logic Simulation


- ▶ A simulator interprets the HDL description, produces readable outputs ex. Timing diagram. Simulation allows detection of functional errors in design Stimulus that tests the functionality of design is test bench

▶ Logic synthesis

- ▶ Deriving a list of components and their interconnections from the HDL description of the digital system. The gate level netlist is used to fabricate the IC.

Using HDLs


Modeling a specification

 

`Z <= '1' when A = '01' else '0'`


Using HDLs... (2)

Simulating a model

 

Using HDLs... (3)

Synthesizing a simulated model

 

Verilog HDL

- ▶ Verilog HDL is
 - ▶ C - like syntax
 - ▶ Initially developed as a simulation tool
 - ▶ With synthesis tools added later used for hardware implementation of the code.
- ▶ History
 - ▶ Developed as proprietary language in 1985
 - ▶ Opened as public domain spec in 1990
 - ▶ Became IEEE standard in 1995

Verilog HDL

- ▶ Verilog constructs are *keywords (lowercase)*
 - ▶ Examples: and, or, wire, input, output
- ▶ One important construct is the *module*
 - ▶ Modules have inputs and outputs
 - ▶ Modules can be built up of Verilog primitives or of user defined sub modules.

Module representation.

- ▶ A logic circuit is specified in the form of a **module**.
(building block)
- ▶ The module is a text description of the circuit layout.
- ▶ Starts with `module` and ends with **endmodule**
- ▶ Module may have inputs, outputs referred to as ports

Module

- ▶ Basic building block of Verilog
- ▶ Describes any one of the three modelling techniques.
- ▶ Gate-level Modelling
 - ▶ using instantiation of primitive gates and user defined modules.
- ▶ Dataflow Modelling
 - ▶ using continuous assignment statements with keyword `assign`
- ▶ Behavioral Modelling
 - ▶ using procedural assignment statements with keyword `always`.

Rules for naming modules

Module Name :

- Can't start with a number
- Should start only with a alphabet or underscore
- Can't contain special characters except “_” (underscore)

Examples

Half_adder , _counter_10 , alu_4bit are **valid** module names

4x1_mux , my@and , alu 8bit are **invalid** module names

Note: Verilog is a **case sensitive** language.

Simple Circuit Notes

- ▶ The module starts with `module` keyword and finishes with `endmodule`.
- ▶ Internal signals are named with `wire`.
- ▶ Comments follow `//`
- ▶ `Input`, `inout` and `output` are ports. These are placed at the start of the module definition.
- ▶ Each statement ends with a semicolon, except `endmodule`.

Primitives

- ▶ Verilog includes gate level primitives

A two input AND gate with inputs x1, x2 and output y is denoted as
and (y,x1,x2)

- ▶ Verilog has all the standard gates

- ▶ **and, nand**

- ▶ **or, nor**

- ▶ **xor, xnor**

- ▶ **not, buf**

GATE LEVEL MODELLING

Example: Simple Circuit Diagram

 


Fig. 3-37 Circuit to Demonstrate HDL

Example: Simple Circuit HDL

```
module smpl_circuit(A,B,C,x,y);  
    input A,B,C;  
    output x,y;  
    wire e;  
    and g1(e,A,B);  
    not g2(y, C);  
    or g3(x,e,y);  
endmodule
```

A vector is specified within square brackets and two numbers separated with colon.

output [0:3] D;


wire [7:0] SUM;

- output vector D with four bits 0 through 3

First number is msb.

- wire vector SUM with eight bits numbered 7 through 0

2-to-4 Line Decoder

 

(a) Logic diagram

| E | A_1 | A_0 | D_0 | D_1 | D_2 | D_3 |
|-----|-------|-------|-------|-------|-------|-------|
| 0 | 0 | 0 | 0 | 1 | 1 | 1 |
| 0 | 0 | 1 | 1 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 | 1 | 1 | 0 |
| 1 | X | X | 1 | 1 | 1 | 1 |

(b) Truth table

$$D_0 = \overline{E} \cdot \overline{A_1} \cdot \overline{A_0}$$

$$D_1 = \overline{E} \cdot \overline{A_1} \cdot A_0$$

$$D_2 = \overline{E} \cdot A_1 \cdot \overline{A_0}$$

$$D_3 = \overline{E} \cdot A_1 \cdot A_0$$

(c) Logic Equations

Fig.3-14 A 2-to-4-Line Decoder

// Gate-level description of a 2-to-4 line decoder

module decoder_g1 (A,B,E,D);

input A,B,E;

output [0:3] D;

wire Anot, Bnot, Enot;

not

 n1 (A1not, A1),

 n2 (A0not, A0),

 n3 (Enot, E);

nand

 n4 (D[0], A1not, A0not, Enot),

 n5 (D[1], A1not, A0, Enot),

 n6 (D[2], A1, A0not, Enot),

 n4 (D[3], A1, A0, Enot);

endmodule

Adding Delays

- ▶ To simulate a circuits real world behavior it is important that propagation delays are included.
- ▶ The units of time for the simulation can be specified with **`timescale`**.
- ▶ **Eg: ``timescale 1us/100ns`**
 - ▶ Default is 1ns with precision of 100ps
- ▶ Component delays are specified as **`#(delay)`**

Simple Circuit with Delay

```
module circuit_with_delay
(A,B,C,x,y);

    input A,B,C;

    output x,y;

    wire e;

    and #(30) g1(e,A,B);

    or  #(20) g3(x,e,y);

    not #(10) g2(y,C);

endmodule
```


Input signals

- ▶ In order to simulate a circuit the input signals need to be known so as to generate an output signal.
- ▶ The input signals are often called the circuit *stimulus*.
- ▶ An HDL module is written to provide the circuit stimulus. This is known as a *testbench*.

Testbench

- ▶ The *testbench* module includes the module to be tested.
- ▶ There are no input or output ports for the testbench.
- ▶ The inputs to the test circuit are defined with **reg** and the outputs with **wire**.
- ▶ The input values are specified with the keyword **initial**
- ▶ A sequence of values can be specified between **begin** and **end**.

Test Bench

 

A Test Bench Block diagram representation

Test Bench

- ❖ A Test Bench is also a Verilog module whose purpose is to generate test patterns for another module.
- ❖ A Test bench doesn't have any input or output ports.
- ❖ A Test bench instantiates the module its going to test.
- ❖ The system tasks are used in test benches.
- ❖ ***\$display , \$monitor , \$time , \$stop, \$finish***

Signal Notation

- ▶ In Verilog signals are generalised to support multi-bit values (e.g. for buses)

- ▶ The notation

A = 1'b0;

- ▶ means signal A is one bit with value zero.

- ▶ The end of the simulation is specified with **\$finish.**

Stimulus module for simple circuit

```
module stimcrt;
  reg A,B,C;
  wire x,y;
  circuit_with_delay cwd(A,B,C,x,y);
  initial
    begin
      A = 1'b0; B = 1'b0; C = 1'b0;
      #100
      A = 1'b1; B = 1'b1; C = 1'b1;
      #100 $finish;
    end
endmodule
```

Effect of delay

| Time (ns) | Input A B C | Output y e x |
|--------------|----------------|-----------------|
| - | 0 0 0 | 1 0 1 |
| - | 1 1 1 | 1 0 1 |
| 10 | 1 1 1 | 0 0 1 |
| 20 | 1 1 1 | 0 0 1 |
| 30 | 1 1 1 | 0 1 0 |
| 40 | 1 1 1 | 0 1 0 |
| 50 | 1 1 1 | 0 1 1 |

Timing Diagram


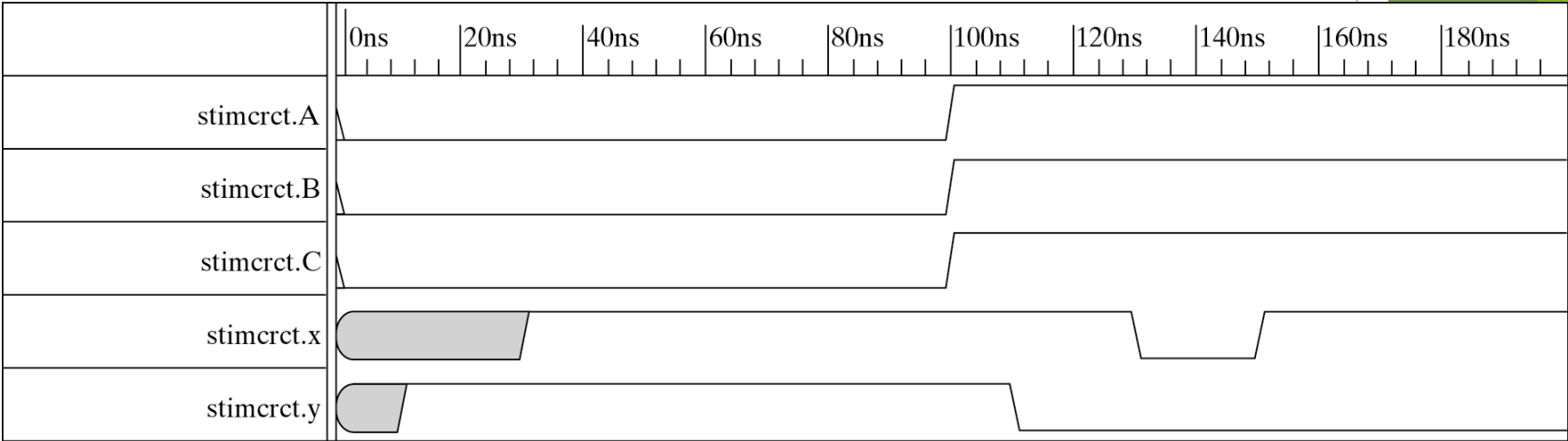


Fig. 3-38 Simulation Output of HDL Example 3-3


- ▶ Two or more modules can be combined to build a hierarchical description of a design.
- ▶ There are two basic types of design methodologies.
 - ▶ Top down : In top-down design, the top level block is defined and then sub-blocks necessary to build the top level block are identified.
 - ▶ Bottom up : Here the building blocks are first identified and then combine to build the top level block.
- ▶ In a top-down design, a 4-bit binary adder is defined as top-level block with 4 full adder blocks. Then we describe two half-adders that are required to create the full adder.
- ▶ In a bottom-up design, the half-adder is defined, then the full adder is constructed and the 4-bit adder is built from the full adders.

- ▶ A bottom-up hierarchical description of a 4-bit adder is described in Verilog as
 - ▶ Half adder is defined by instantiating primitive gates.
 - ▶ Then define the full adder by instantiating two half-adders.
 - ▶ Finally the third module describes 4 bit adder by instantiating 4 full adders.
- ▶ **Note:** In Verilog, one module definition cannot be placed within another module description.

4 bit Full Adder

 
 
$$(a) \begin{aligned} S &= xy' + x'y \\ C &= xy \end{aligned}$$



$$(b) \begin{aligned} S &= x \oplus y \\ C &= xy \end{aligned}$$

Fig. 4-5 Implementation of Half-Adder

4 bit Full Adder

 


Fig. 4-8 Implementation of Full Adder with Two Half Adders and an OR Gate

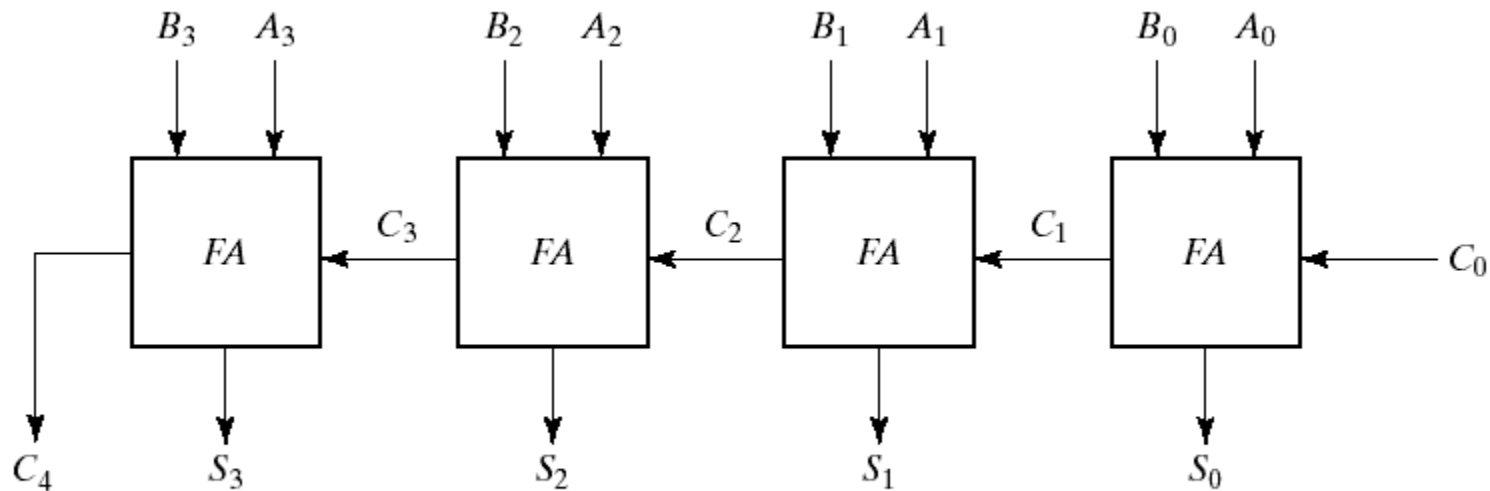


Fig. 4-9 4-Bit Adder

4 bit Full Adder

//Gate-level hierarchical description of 4-bit adder

```
module halfadder (S,C,x,y);
```

```
    input x,y;
```

```
    output S,C;
```

```
//Instantiate primitive gates
```

```
    xor (S,x,y);
```

```
    and (C,x,y);
```

```
endmodule
```

```
module fulladder (S,C,x,y,z);
```

```
    input x,y,z;
```

```
    output S,C;
```

```
    wire S1,D1,D2; //Outputs of first XOR and two AND gates
```

```
//Instantiate the halfadder
```

```
    halfadder HA1 (S1,D1,x,y),
```

```
                HA2 (S,D2,S1,z);
```

```
    or g1(C,D2,D1);
```

```
endmodule
```

 


Fig. 4-8 Implementation of Full Adder with Two Half Adders and an OR Gate

```
//Description of 4-bit adder (see Fig 4-9)
module _4bit_adder (S,C4,A,B,C0);
    input [3:0] A,B;
    input C0;
    output [3:0] S;
    output C4;
    wire C1,C2,C3; //Intermediate carries
    //Instantiate the fulladder
    fulladder FA0 (S[0],C1,A[0],B[0],C0),
               FA1 (S[1],C2,A[1],B[1],C1),
               FA2 (S[2],C3,A[2],B[2],C2),
               FA3 (S[3],C4,A[3],B[3],C3);
endmodule
```

4-to-1 Multiplexer

 


Fig. 3-19 4-to-1-Line Multiplexer

4-to-1 Multiplexer

```
// 4-to-1 Line Multiplexer: Structural Verilog Description
// (See Figure 3-19 for logic diagram)
module multiplexer_4_to_1_st_v(S, D, Y);
    input [1:0] S;
    input [3:0] D;
    output Y;

    wire [1:0] not_S;
    wire [0:3] N;

    not
        gn0(not_S[0], S[0]),
        gn1(not_S[1], S[1]);

    and
        g0(N[0], not_S[1], not_S[0], D[0]),
        g1(N[1], not_S[1], S[0], D[1]),
        g2(N[2], S[1], not_S[0], D[2]),
        g3(N[3], S[1], S[0], D[3]);

    or go(Y, N[0], N[1], N[2], N[3]);

endmodule
```

// 1
// 2
// 3
// 4
// 5
// 6
// 7
// 8
// 9
// 10
// 11
// 12
// 13
// 14
// 15
// 16
// 17
// 18
// 19
// 20
// 21
// 22
// 23

Fig. 3-45 Structural Verilog Description of a 4-to-1 Line Multiplexer

DATA FLOW MODELLING

Dataflow modelling

- ▶ Another level of abstraction is to model dataflow.
- ▶ Dataflow modeling uses a number of operators that act on operands to produce desired results.
- ▶ Verilog HDL provides about 30 operator types.
- ▶ In dataflow models, signals are continuously assigned values using the **assign** keyword.

Dataflow Modeling

- ▶ A continuous assignment is a statement that assigns a value to a net.
- ▶ The value assigned to the net is specified by an expression that uses operands and operators.
- ▶ For ex: assign $Y = (A \&B) \mid (C \&D)$
- ▶ **assign** can be used with Boolean expressions.
 - ▶ Verilog uses & (and), \mid (or), \wedge (xor) and \sim (not)
- ▶ Logic expressions and binary arithmetic are also possible.

Simple Circuit Boolean Expression

 


Fig. 3-37 Circuit to Demonstrate HDL

$$x = A.B + C \quad \text{---}$$

$$y = C \text{---}$$

Boolean Expressions

//Circuit specified with Boolean equations

```
module circuit_bln (A,B,C,x,y);
```

```
    input A,B,C;
```


```
    output x,y;
```

```
    assign x = (A &B) | (~C);
```

```
    assign y = ~C ;
```

```
endmodule
```

2-to-4 Line Decoder

 

(a) Logic diagram

| E | A_1 | A_0 | D_0 | D_1 | D_2 | D_3 |
|-----|-------|-------|-------|-------|-------|-------|
| 0 | 0 | 0 | 0 | 1 | 1 | 1 |
| 0 | 0 | 1 | 1 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 | 1 | 1 | 0 |
| 1 | X | X | 1 | 1 | 1 | 1 |

(b) Truth table

$$D_0 = \overline{E} \overline{A_1} \overline{A_0}$$

$$D_1 = \overline{E} \overline{A_1} A_0$$

$$D_2 = \overline{E} A_1 \overline{A_0}$$

$$D_3 = \overline{E} A_1 A_0$$

(c) Logic Equations

Fig.3-14 A 2-to-4-Line Decoder

Dataflow Modeling

//Dataflow description of a 2-to-4-line decoder

//See Fig.4-19

```
module decoder_df (A,B,E,D);  
    input A,B,E;  
    output [0:3] D;  
    assign D[0] = ~(~A1 & ~A0 & ~E),  
           D[1] = ~(~A1 & A0 & ~E),  
           D[2] = ~(A1 & ~A0 & ~E),  
           D[3] = ~(A1 & A0 & ~E);  
endmodule
```

4 bit Full Adder

 


Fig. 4-8 Implementation of Full Adder with Two Half Adders and an OR Gate

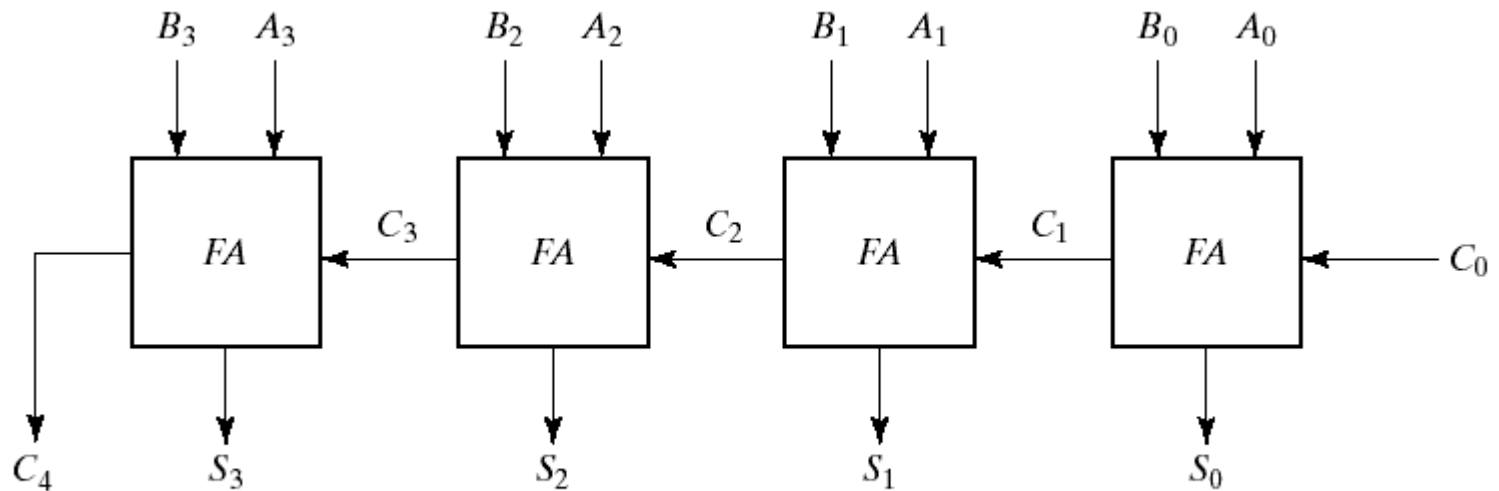


Fig. 4-9 4-Bit Adder

Dataflow Modeling

```
//Dataflow description of 4-bit adder  
module binary_adder (A,B,Cin,SUM,Cout);  
    input [3:0] A,B;  
    input Cin;  
    output [3:0] SUM;  
    output Cout;  
    assign {Cout,SUM} = A + B + Cin;  
endmodule
```

Dataflow Modeling

- ▶ The addition logic of 4 bit adder is described by a single statement using the operators of addition and concatenation.
- ▶ The plus symbol (+) specifies the binary addition of the 4 bits of *A* with the 4 bits of *B* and the one bit of *Cin*.
- ▶ The target output is the concatenation of the output carry *Cout* and the four bits of *SUM*.
- ▶ Concatenation of operands is expressed within braces and a comma separating the operands. Thus, $\{Cout, SUM\}$ represents the 5-bit result of the addition operation.


- ▶ Dataflow modelling provides means of describing combinational circuit by function rather than gate structure.
- ▶ A verilog HDL Synthesis tool can accept this module as input and can provide a netlist of a circuit equivalent.

Dataflow Modeling

```
//Dataflow description of a 4-bit comparator.  
module magcomp (A,B,ALTB,AGTB,AEQB);  
    input [3:0] A,B;  
    output ALTB,AGTB,AEQB;  
    assign ALTB = (A < B),  
           AGTB = (A > B),  
           AEQB = (A == B);  
endmodule
```



Multiplexer

  - ▶ Multiplexer is a combinational circuit where an input is chosen by a select signal.
 - ▶ Two input mux
 - ▶ output = A if select = 1
 - ▶ output = B if select = 0



Two Input Multiplexor

- A two-input mux is actually a three input device.



$$x = A.s + B.s \quad -$$

| s | A | B | x |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 |

Dataflow description of 2-input Mux

- Conditional operator `?:` takes three operands:

`condition? true_expression : false_expression`

```
module mux2x1_df (A,B,select,OUT);  
    input A,B,select;  
    output OUT;  
    assign OUT = select ? A : B;  
endmodule
```

Behavioral modelling

Behavioral Modeling

- ▶ Behavioral modeling represents digital circuits at a **functional** and **algorithmic** level.
- ▶ mostly to describe sequential circuits, but can also be used to describe combinational circuits.
- ▶ uses the keyword **always** followed by a list of procedural assignment statements.
- ▶ The target output of procedural assignment statements must be of the **reg** data type.
- ▶ A **reg** data type retains its value until a new value is assigned.

Behavioral Modelling

- ▶ Behavioral models place procedural statements in a block after the **always** keyword.
- ▶ The **always** keyword takes a list of variables. The block of statements is executed whenever one of the variables changes.
- ▶ The target variables are of type **reg**. This type retains its value until a new value is assigned.

Behavioral Modeling


- ▶ The procedural assignment statements inside the **always** block are executed every time there is a change in any of the variable listed after the @ symbol. (Note that there is no “;” at the end of **always** statement)

Behavioral description of 2-input mux

```
module  
mux2x1_bh(A,B,select,OUT);  
  input A,B,select;  
  output OUT;  
  reg OUT;  
  always @ (select or A or B)  
    if (select == 1)  
      OUT = A;  
    else OUT = B;  
endmodule
```


Behavioral Modelling

4-to-1 line
multiplexer

 

(a) Logic diagram

| s_1 | s_0 | Y |
|-------|-------|-------|
| 0 | 0 | I_0 |
| 0 | 1 | I_1 |
| 1 | 0 | I_2 |
| 1 | 1 | I_3 |

(b) Function table

Behavioural Modelling Example

```
module mux_4X1 (y, s, d ) ;  
input    [3:0] d ; // four input lines  
modeled as a bus  
Input    [1:0] s ; // select lines bundled as  
a bus  
output reg y ;  
always @ ( * )  
begin  
  case (s)  
    2`b00 : y = d[0] ;  
    2`b01 : y = d[1] ;  
    2`b10 : y = d[2] ;  
    2`b11 : y = d[3] ;  
  default : y = 1`bz ;  
  endcase  
end  
endmodule
```

Behavioural Modelling: Case statement

- **case** statement can have one *default* statement.
- **casex** will treat both x and z as don't care conditions
- **casez** will treat only z as don't care condition.
- A ? Can also be used instead of z
- If any of the bits in the case expression or case item expression is a don't-care value then that bit position will be ignored.

Behavioral Modeling


- ▶ In 4-to-1 line multiplexer, the select input is defined as a 2-bit vector and output y is declared as a reg data.
- ▶ The always block has a sequential block enclosed between the keywords case and endcase.
- ▶ The block is executed whenever any of the inputs listed after the @ symbol changes in value.

Clocked circuits

- ▶ In case of sequential design which are sensitive to edge of the clocks we use **posedge** or **negedge**
- ▶ **Posedge**= positive edge triggered
- ▶ **negedge**= negative edge triggered

Behavioural Modelling Example
 
```
module dff_ (q,clk,reset,d);  
input clk,reset,d ;  
output reg q ;  
always @(posedge clk)  
begin  
  if(reset)  
    q <= 0 ;  
  else  
    q <= d ;  
  end  
endmodule
```



TRY IT OUT

- ▶ Can you specify edge sensitive and level sensitive input in a single sensitivity list statement in a single always block? i.e. can we have a statement `always @(d or posedge (clk))`

HDL Summary

- ▶ Hardware Description Languages allow fast design and verification of digital circuits.
- ▶ Accurate simulation and testing requires delays and inputs to be specified.
- ▶ There are three different levels of abstraction for modelling circuits.